

Multisim Circuit Experiment Report

Generated automatically by Multisim MCP

Experiment overview

5V voltage divider Reproducibility - Multisim design: circuit.ms14 - Analysis commands: op - Simulation succeeded: True - Points: 1 - Columns: V(in), V(out), I(v1) Circuit netlist spice V1 in 0 5 R1 in out 10k R2 out 0 10k .end Artifacts - Editable circuit: circuit.ms14 - Schematic: ![schematic](schematic.png) - Data: data.csv - Plot: ![plot](plot.svg) Data preview V(in) V(out) I(v1) --- --- --- 5 2.5 -0.00025 Automatic measurements signal first last min max mean --- ---: ---: ---: ---: ---: V(in) 5 5 5 5 5 V(out) 2.5 2.5 2.5 2.5 2.5 I(v1) -0.00025 -0.00025 -0.00025 -0.00025 -0.00025 Diagnostics - Timed out: False - Last error: Generated by the unofficial Multisim MCP. Verify safety-critical results independently.

Data summary

V(in): N=1, min=5, max=5, mean=5
V(out): N=1, min=2.5, max=2.5, mean=2.5
I(v1): N=1, min=-0.00025, max=-0.00025, mean=-0.00025

Requirement verification

No verification requirements were provided.

Circuit netlist

```
V1 in 0 5
R1 in out 10k
R2 out 0 10k
.end
```

Reproducibility

manifest.json contains SHA-256 hashes for all artifacts.